In Class Exercise 2 – Julio Tain Sueiras Student ID:991327201

1.Truth Tables

X	у	$\overline{\mathbf{y}}$	y+x	$x(\overline{y}+x)$
1	1	0	1	1
1	0	1	1	1
0	1	0	0	0
0	0	1	1	0

2.Truth Tables

a	b	С	b	ъс	a+(bc)		
1	1	1	0	0	1		
1	1	0	0	0	1		
1	0	1	1	1	1		
1	0	0	1	0	1		
0	1	1	0	0	0		
0	1	0	0	0	0		
0	0	1	1	1	1		
0	0	0	1	0	0		

3.Truth Tables

a	b	С	b+c	a+(b+c)	b(a+(b+c))
1	1	1	1	1	1
1	1	0	1	1	1
1	0	1	1	1	0
1	0	0	0	1	0
0	1	1	1	1	1
0	1	0	1	1	1
0	0	1	1	1	0
0	0	0	0	0	0

4.Truth Tables

A	В	С	AB	AB+C	AB+C
1	1	1	1	1	0
1	1	0	1	1	0
1	0	1	0	1	0
1	0	0	0	0	1
0	1	1	0	1	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	0	0	1


5.Truth Tables

A	В	С	AB	\overline{C}	AB+C
1	1	1	1	0	1
1	1	0	1	1	1
1	0	1	0	0	0
1	0	0	0	1	1
0	1	1	0	0	0
0	1	0	0	1	1
0	0	1	0	0	0
0	0	0	0	1	1

5.Truth Tables

٠. ـ	<u></u>							
A	В	С	\overline{C}	AB	ĀB	AB+ AB	$\overline{C}(AB+\overline{AB})$	
1	1	1	0	1	0	1	0	
1	1	0	1	1	0	1	1	
1	0	1	0	0	1	1	0	
1	0	0	1	0	1	1	1	
0	1	1	0	0	1	1	0	
0	1	0	1	0	1	1	1	
0	0	1	0	0	1	1	0	
0	0	0	1	0	1	1	1	

Logic Gates

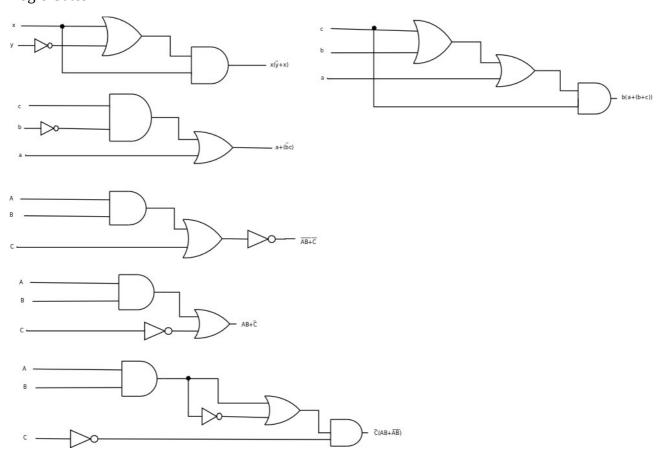

Part 2.
1.
$$\overline{c}$$
+(ab) 2. $\overline{r}(\overline{pq}$ +rp) 3. $\overline{r}(\overline{p}$ +q) 4. \overline{q} r+p